The circuit of capacitors connected to a battery is at equilibrium.

- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the voltage V_3 across capacitor C_3 .
- (c) Find the the charge Q_2 on capacitor C_2 .



Solution:

(a)
$$C_{12} = C_1 + C_2 = 3\mu F$$
, $C_{eq} = \left(\frac{1}{C_{12}} + \frac{1}{C_3}\right)^{-1} = 1.5\mu F$.

(b)
$$Q_3 = Q_{12} = Q_{eq} = C_{eq}(8V) = 12\mu C$$

 $\Rightarrow V_3 = \frac{Q_3}{C_3} = \frac{12\mu C}{3\mu F} = 4V.$

(c) $Q_2 = V_2 C_2 = 8 \mu C.$

Consider the electrical circuit shown.

- (a) Find the equivalent resistance R_{eq} .
- (b) Find the current I_3 through resistor R_3 .



Solution:

(a)
$$R_{36} = \left(\frac{1}{R_3} + \frac{1}{R_6}\right)^{-1} = 2\Omega, \quad R_{eq} = R_2 + R_{36} = 4\Omega.$$

(b) $I_2 = I_{36} = \frac{12V}{R_{eq}} = 3A$
 $\Rightarrow V_3 = V_{36} = I_{36}R_{36} = 6V \quad \Rightarrow I_3 = \frac{V_3}{R_3} = 2A.$

This RC circuit has been running for a long time.

- (a) Find the current I_2 through the resistor R_2 .
- (b) Find the voltage V_C across the capacitor.



Solution:

(a)
$$I_C = 0$$
, $I_2 = \frac{\mathcal{E}}{R_1 + R_2} = \frac{12V}{6\Omega} = 2A$.
(b) $V_C = V_2 = I_2 R_2 = (2A)(4\Omega) = 8V$.





Consider a charged particle moving in a uniform magnetic field as shown. The velocity is in *y*-direction and the magnetic field in the *yz*-plane at 30° from the *y*-direction.

- (a) Find the direction of the magnetic force acting on the particle.
- (b) Find the magnitude of the magnetic force acting on the particle.



Solution:

- (a) Use the right-hand rule: positive *x*-direction (front, out of page).
- (b) $F = qvB\sin 30^\circ = (5 \times 10^{-9} \text{C})(3\text{m/s})(4 \times 10^{-3} \text{T})(0.5) = 3 \times 10^{-11} \text{N}.$