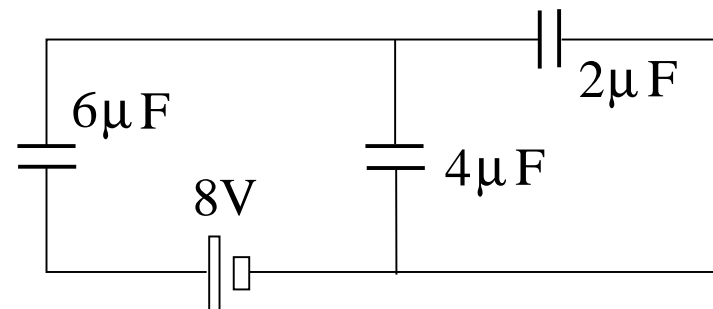


Unit Exam II: Problem #1 (Spring '16)



The circuit of capacitors connected to a battery is at equilibrium.

- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the total energy U stored in the three capacitors.
- (c) Find the charge Q_6 on the capacitor on the left.
- (d) Find the voltages V_2 and V_4 across the two capacitors on the right.



Unit Exam II: Problem #1 (Spring '16)




The circuit of capacitors connected to a battery is at equilibrium.

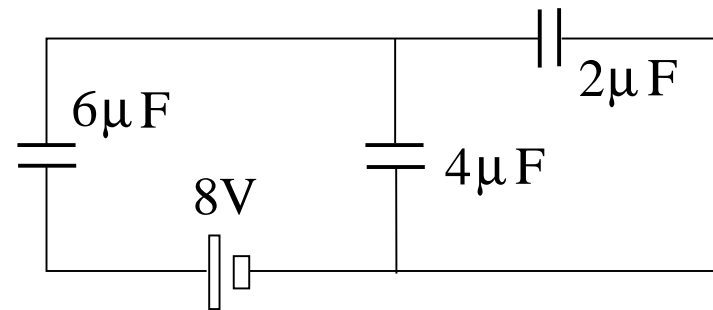- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the total energy U stored in the three capacitors.
- (c) Find the charge Q_6 on the capacitor on the left.
- (d) Find the voltages V_2 and V_4 across the two capacitors on the right.

Solution:

$$(a) \quad C_{eq} = \left(\frac{1}{2\mu\text{F} + 4\mu\text{F}} + \frac{1}{6\mu\text{F}} \right)^{-1} = 3\mu\text{F}.$$



Unit Exam II: Problem #1 (Spring '16)




The circuit of capacitors connected to a battery is at equilibrium.

- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the total energy U stored in the three capacitors.
- (c) Find the charge Q_6 on the capacitor on the left.
- (d) Find the voltages V_2 and V_4 across the two capacitors on the right.

Solution:

$$(a) \quad C_{eq} = \left(\frac{1}{2\mu\text{F} + 4\mu\text{F}} + \frac{1}{6\mu\text{F}} \right)^{-1} = 3\mu\text{F}.$$
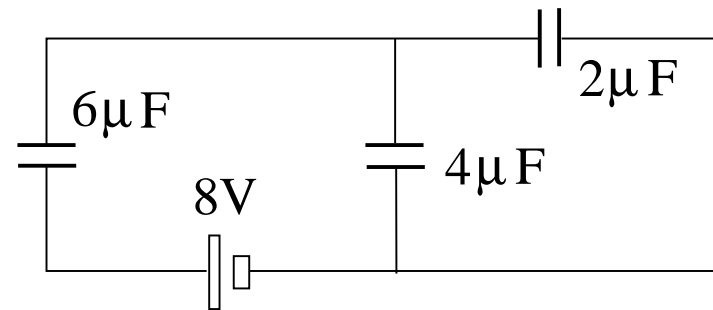
$$(b) \quad U = \frac{1}{2}(3\mu\text{F})(8\text{V})^2 = 96\mu\text{J}.$$



Unit Exam II: Problem #1 (Spring '16)



The circuit of capacitors connected to a battery is at equilibrium.


- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the total energy U stored in the three capacitors.
- (c) Find the charge Q_6 on the capacitor on the left.
- (d) Find the voltages V_2 and V_4 across the two capacitors on the right.

Solution:

$$(a) \quad C_{eq} = \left(\frac{1}{2\mu\text{F} + 4\mu\text{F}} + \frac{1}{6\mu\text{F}} \right)^{-1} = 3\mu\text{F}.$$

$$(b) \quad U = \frac{1}{2}(3\mu\text{F})(8\text{V})^2 = 96\mu\text{J}.$$
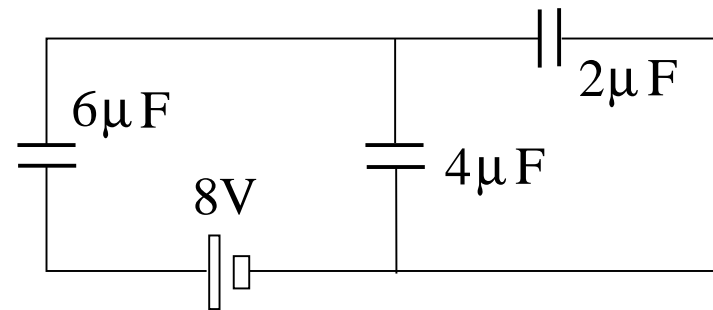
$$(c) \quad Q_6 = (8\text{V})(3\mu\text{F}) = 24\mu\text{C}.$$



Unit Exam II: Problem #1 (Spring '16)



The circuit of capacitors connected to a battery is at equilibrium.

- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the total energy U stored in the three capacitors.
- (c) Find the charge Q_6 on the capacitor on the left.
- (d) Find the voltages V_2 and V_4 across the two capacitors on the right.


Solution:

$$(a) \quad C_{eq} = \left(\frac{1}{2\mu\text{F} + 4\mu\text{F}} + \frac{1}{6\mu\text{F}} \right)^{-1} = 3\mu\text{F}.$$

$$(b) \quad U = \frac{1}{2}(3\mu\text{F})(8\text{V})^2 = 96\mu\text{J}.$$

$$(c) \quad Q_6 = (8\text{V})(3\mu\text{F}) = 24\mu\text{C}.$$
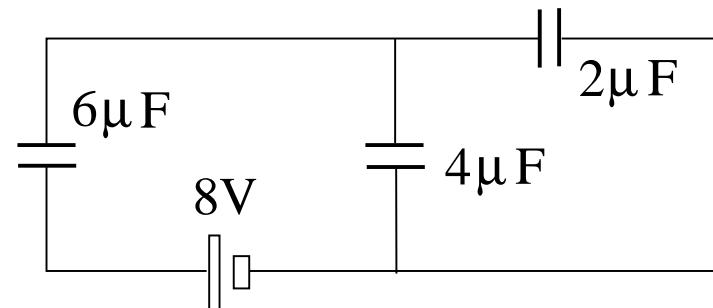
$$(d) \quad V_2 = V_4 = \frac{1}{2}(8\text{V}) = 4\text{V}.$$




Unit Exam II: Problem #2 (Spring '16)



Consider the electrical circuit shown.

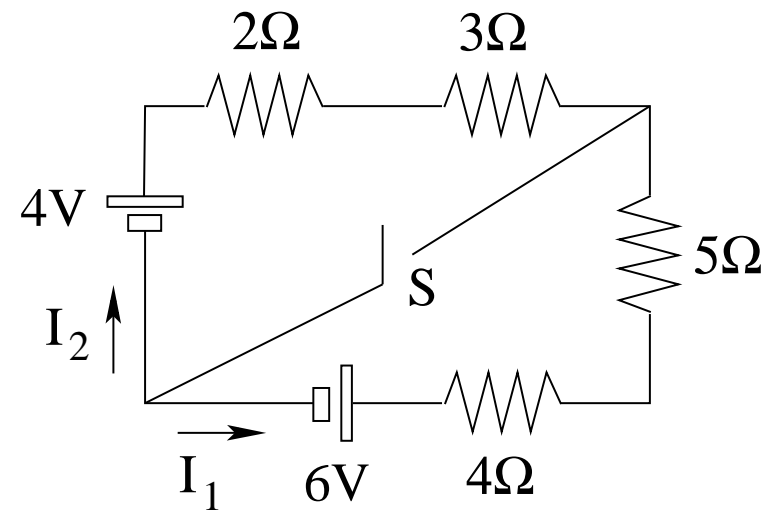- (a) Find the current I_1 when the switch S is open.
- (b) Find the currents I_1 and I_2 when the switch S is closed.



Unit Exam II: Problem #2 (Spring '16)




Consider the electrical circuit shown.

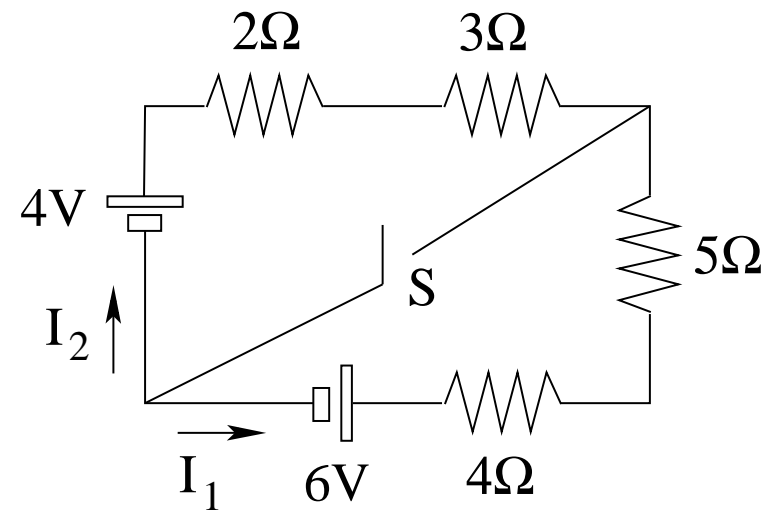- (a) Find the current I_1 when the switch S is open.
- (b) Find the currents I_1 and I_2 when the switch S is closed.

Solution:

$$(a) \quad I_1 = \frac{6V - 4V}{4\Omega + 5\Omega + 3\Omega + 2\Omega} = 0.143A.$$



Unit Exam II: Problem #2 (Spring '16)




Consider the electrical circuit shown.

- (a) Find the current I_1 when the switch S is open.
- (b) Find the currents I_1 and I_2 when the switch S is closed.

Solution:

$$(a) \quad I_1 = \frac{6V - 4V}{4\Omega + 5\Omega + 3\Omega + 2\Omega} = 0.143A.$$
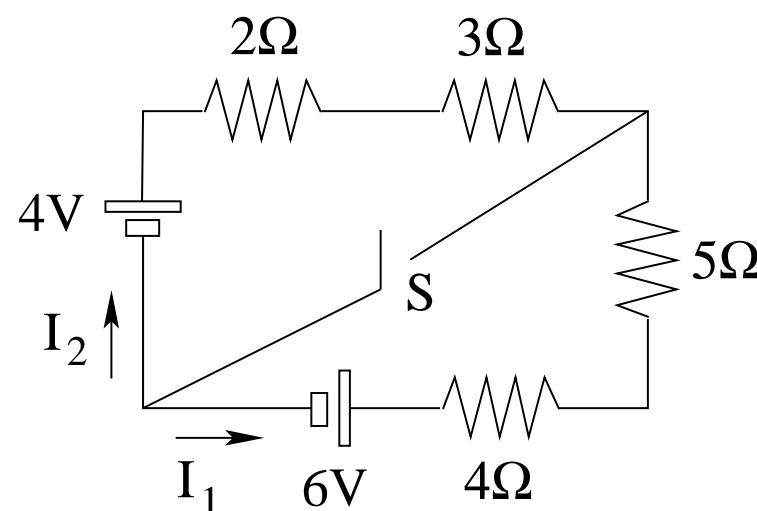
$$(b) \quad I_1 = \frac{6V}{4\Omega + 5\Omega} = 0.667A, \quad I_2 = \frac{4V}{3\Omega + 2\Omega} = 0.8A.$$




Unit Exam II: Problem #3 (Spring '15)



This RC circuit has been running for a long time with the switch open.

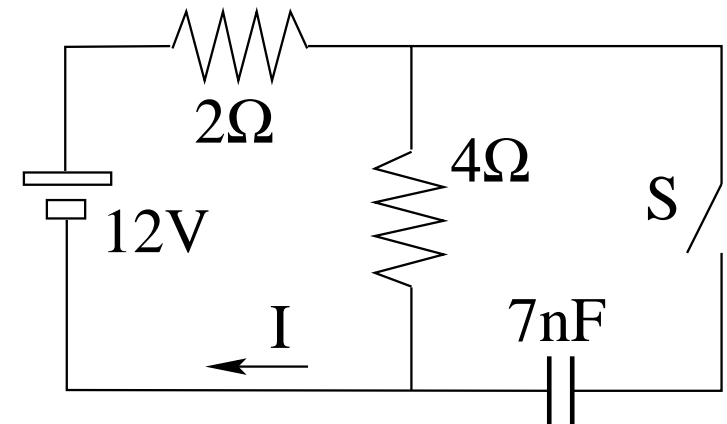- (a) Find the current I while the switch is still open.
- (b) Find the current I right after the switch has been closed.
- (c) Find the current I a long time later.
- (d) Find the charge Q on the capacitor also a long time later.



Unit Exam II: Problem #3 (Spring '15)




This RC circuit has been running for a long time with the switch open.

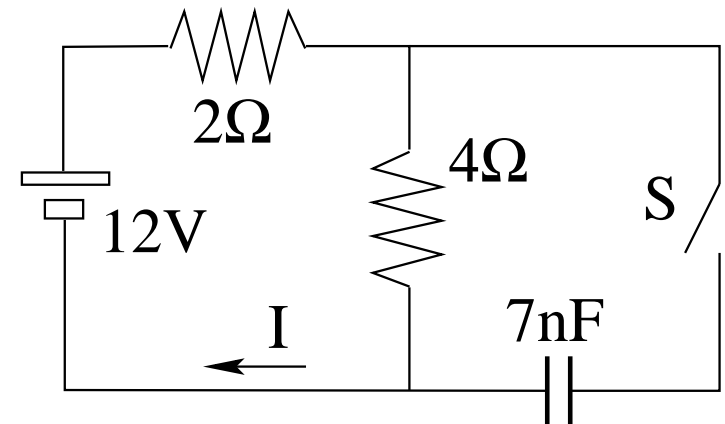- (a) Find the current I while the switch is still open.
- (b) Find the current I right after the switch has been closed.
- (c) Find the current I a long time later.
- (d) Find the charge Q on the capacitor also a long time later.

Solution:

$$(a) \quad I = \frac{12V}{2\Omega + 4\Omega} = 2A.$$



Unit Exam II: Problem #3 (Spring '15)




This RC circuit has been running for a long time with the switch open.

- (a) Find the current I while the switch is still open.
- (b) Find the current I right after the switch has been closed.
- (c) Find the current I a long time later.
- (d) Find the charge Q on the capacitor also a long time later.

Solution:

$$(a) \quad I = \frac{12V}{2\Omega + 4\Omega} = 2A.$$
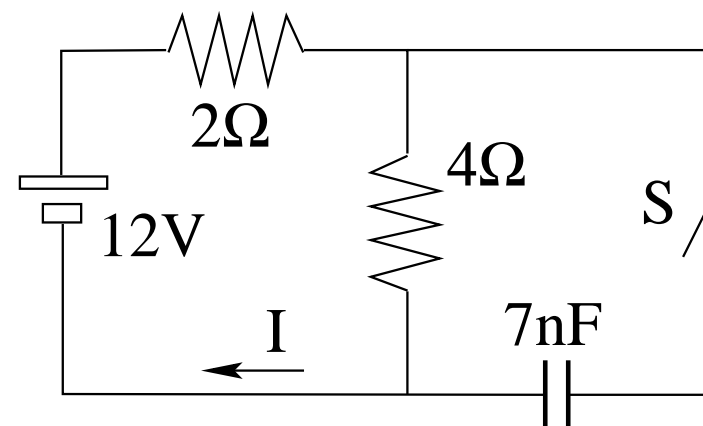
$$(b) \quad I = \frac{12V}{2\Omega} = 6A.$$



Unit Exam II: Problem #3 (Spring '15)



This RC circuit has been running for a long time with the switch open.


- (a) Find the current I while the switch is still open.
- (b) Find the current I right after the switch has been closed.
- (c) Find the current I a long time later.
- (d) Find the charge Q on the capacitor also a long time later.

Solution:

$$(a) \quad I = \frac{12V}{2\Omega + 4\Omega} = 2A.$$

$$(b) \quad I = \frac{12V}{2\Omega} = 6A.$$
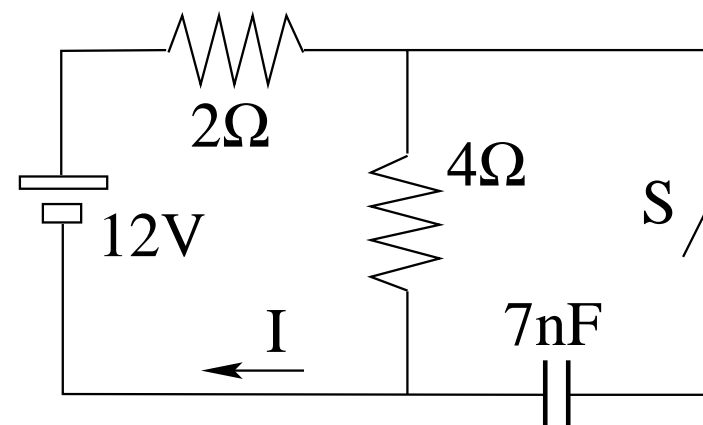
$$(c) \quad I = \frac{12V}{2\Omega + 4\Omega} = 2A.$$



Unit Exam II: Problem #3 (Spring '15)



This RC circuit has been running for a long time with the switch open.

- (a) Find the current I while the switch is still open.
- (b) Find the current I right after the switch has been closed.
- (c) Find the current I a long time later.
- (d) Find the charge Q on the capacitor also a long time later.

Solution:

$$(a) \quad I = \frac{12V}{2\Omega + 4\Omega} = 2A.$$

$$(b) \quad I = \frac{12V}{2\Omega} = 6A.$$

$$(c) \quad I = \frac{12V}{2\Omega + 4\Omega} = 2A.$$

$$(d) \quad Q = (8V)(7nF) = 56nC.$$

