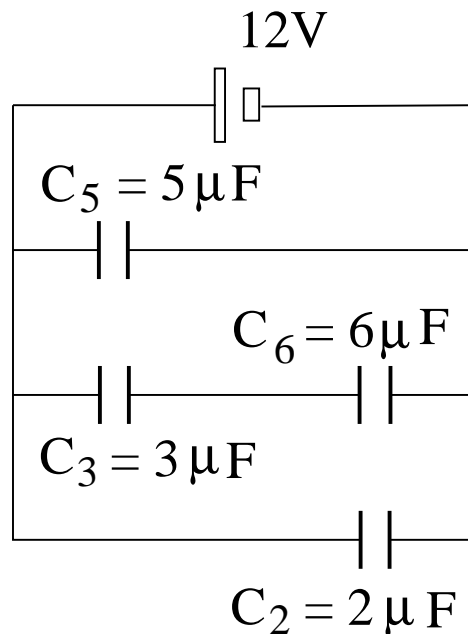


Unit Exam II: Problem #1 (Fall '16)




The capacitors (initially discharged) have been connected to the battery. The circuit is now at equilibrium. Find ...

- (a) the voltage V_2 across capacitor C_2 ,
- (b) the energy U_5 on capacitor C_5 ,
- (c) the charge Q_3 on capacitor C_3 ,
- (d) the equivalent capacitance C_{eq} .



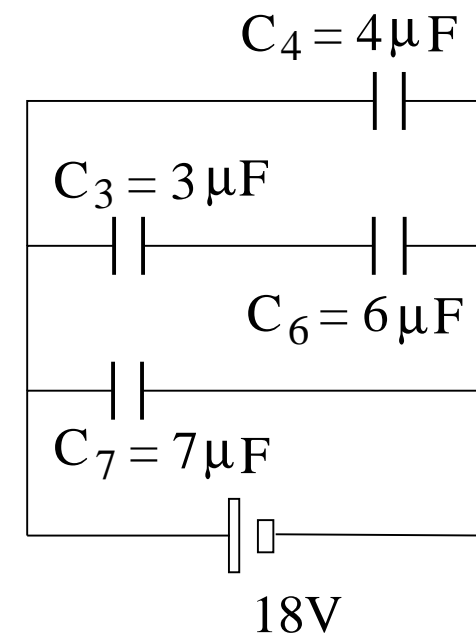- (a) the voltage V_4 across capacitor C_4 ,
- (b) the energy U_7 on capacitor C_7 ,
- (c) the charge Q_6 on capacitor C_6 ,
- (d) the equivalent capacitance C_{eq} .



Unit Exam II: Problem #1 (Fall '16)



The capacitors (initially discharged) have been connected to the battery. The circuit is now at equilibrium. Find ...

- (a) the voltage V_2 across capacitor C_2 ,
- (b) the energy U_5 on capacitor C_5 ,
- (c) the charge Q_3 on capacitor C_3 ,
- (d) the equivalent capacitance C_{eq} .

- (a) the voltage V_4 across capacitor C_4 ,
- (b) the energy U_7 on capacitor C_7 ,
- (c) the charge Q_6 on capacitor C_6 ,
- (d) the equivalent capacitance C_{eq} .

Solution:

- (a) $V_2 = 12\text{V}$.
- (b) $U_5 = \frac{1}{2}(5\mu\text{F})(12\text{V})^2 = 360\mu\text{J}$.
- (c) $C_{36} = 2\mu\text{F}$
 $\Rightarrow Q_3 = Q_{36} = (12\text{V})(2\mu\text{F}) = 24\mu\text{C}$.
- (d) $C_{eq} = C_5 + C_{36} + C_2 = 9\mu\text{F}$.


- (a) $V_4 = 18\text{V}$.
- (b) $U_7 = \frac{1}{2}(7\mu\text{F})(18\text{V})^2 = 1134\mu\text{J}$.
- (c) $C_{36} = 2\mu\text{F}$
 $\Rightarrow Q_6 = Q_{36} = (18\text{V})(2\mu\text{F}) = 36\mu\text{C}$.
- (d) $C_{eq} = C_4 + C_{36} + C_7 = 13\mu\text{F}$.

Unit Exam II: Problem #2 (Fall '16)




This resistor circuit is in a state of steady currents. Find ...

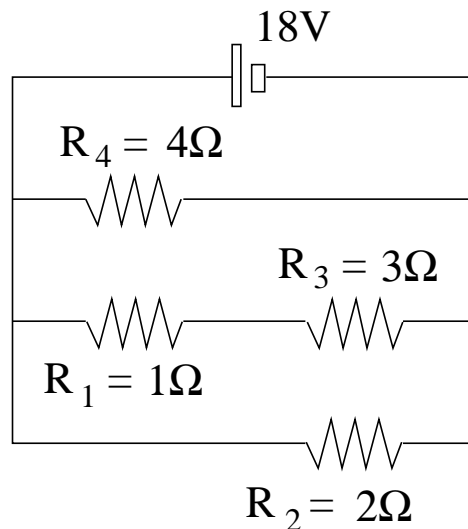- (a) the voltage V_2 across resistor R_2 ,
- (b) the power P_4 dissipated in resistor R_4 ,
- (c) the current I_3 flowing through resistor R_3
- (d) the equivalent resistance R_{eq} .



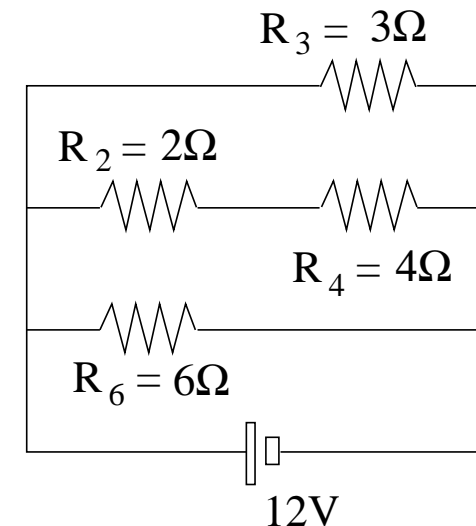- (a) the voltage V_3 across resistor R_3 ,
- (b) the power P_6 dissipated in resistor R_6 ,
- (c) the current I_4 flowing through resistor R_4 ,
- (d) the equivalent resistance R_{eq} .



Unit Exam II: Problem #2 (Fall '16)



This resistor circuit is in a state of steady currents. Find ...

- (a) the voltage V_2 across resistor R_2 ,
- (b) the power P_4 dissipated in resistor R_4 ,
- (c) the current I_3 flowing through resistor R_3
- (d) the equivalent resistance R_{eq} .

- (a) the voltage V_3 across resistor R_3 ,
- (b) the power P_6 dissipated in resistor R_6 ,
- (c) the current I_4 flowing through resistor R_4 ,
- (d) the equivalent resistance R_{eq} .

Solution:

- (a) $V_2 = 18\text{V}$.
- (b) $P_4 = \frac{18\text{V}^2}{4\Omega} = 81\text{W}$.
- (c) $I_3 = \frac{18\text{V}}{3\Omega + 1\Omega} = 4.5\text{A}$.
- (d) $R_{eq} = \left(\frac{1}{4\Omega} + \frac{1}{1\Omega + 3\Omega} + \frac{1}{2\Omega} \right)^{-1} = 1\Omega$.



- (a) $V_3 = 12\text{V}$
- (b) $P_6 = \frac{12\text{V}^2}{6\Omega} = 24\text{W}$.
- (c) $I_4 = \frac{12\text{V}}{2\Omega + 4\Omega} = 2\text{A}$.
- (d) $R_{eq} = \left(\frac{1}{3\Omega} + \frac{1}{2\Omega + 4\Omega} + \frac{1}{6\Omega} \right)^{-1} = 1.5\Omega$

Unit Exam II: Problem #3 (Fall '16)



This two-loop resistor circuit is in a state of steady currents. Find ...

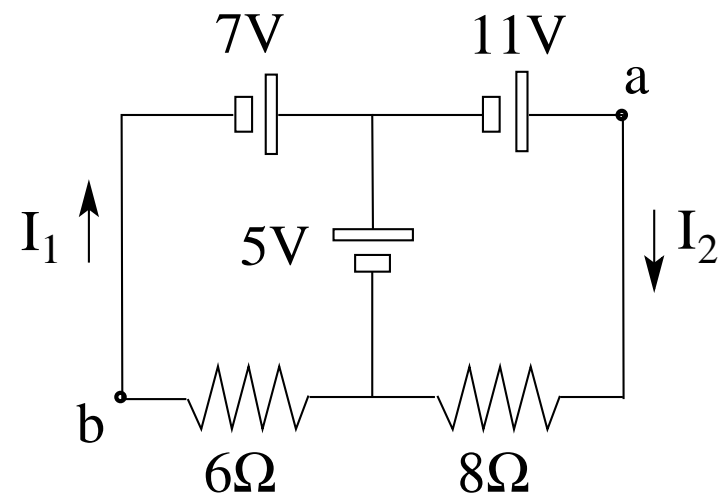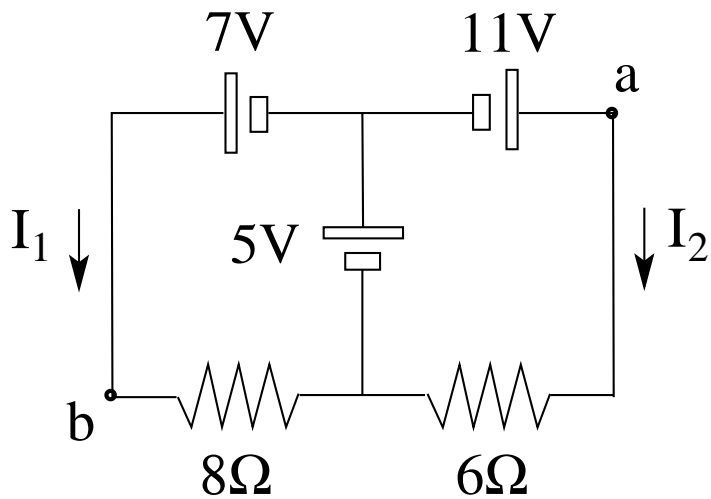- (a) the current I_1 ,
- (b) the current I_2 ,
- (c) the potential difference $V_a - V_b$.





Unit Exam II: Problem #3 (Fall '16)



This two-loop resistor circuit is in a state of steady currents. Find ...

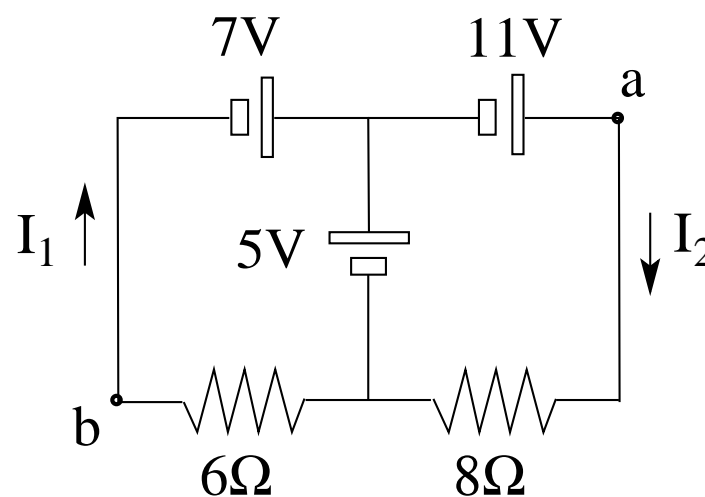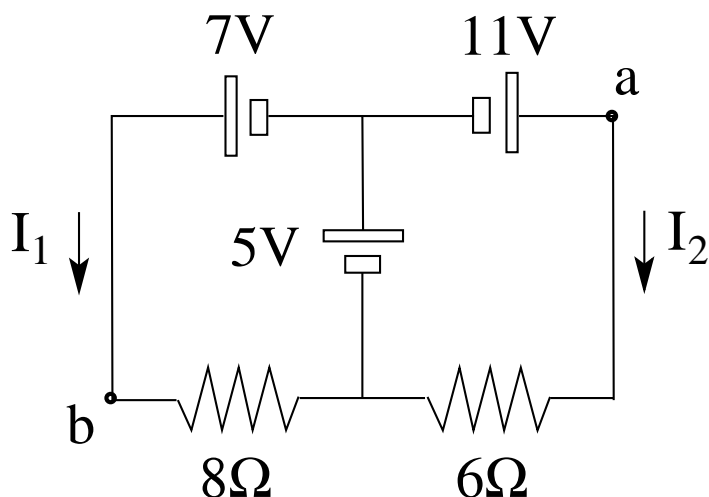- (a) the current I_1 ,
- (b) the current I_2 ,
- (c) the potential difference $V_a - V_b$.



Solution:

$$(a) \quad I_1 = \frac{5V + 7V}{8\Omega} = +1.5A.$$

$$(b) \quad I_2 = \frac{5V + 11V}{6\Omega} = +2.67A.$$

$$(c) \quad V_a - V_b = -7V + 11V = +4V.$$

$$(a) \quad I_1 = \frac{7V - 5V}{6\Omega} = +0.333A.$$

$$(b) \quad I_2 = \frac{5V + 11V}{8\Omega} = +2A.$$

$$(c) \quad V_a - V_b = 7V + 11V = +18V.$$