


## Unit Exam II: Problem #1 (Spring '18)



The circuit shown has reached equilibrium.

The specifications are  $\mathcal{E} = 12\text{V}$  [18V],  $C_1 = C_2 = C_3 = 5\text{nF}$  [4nF]

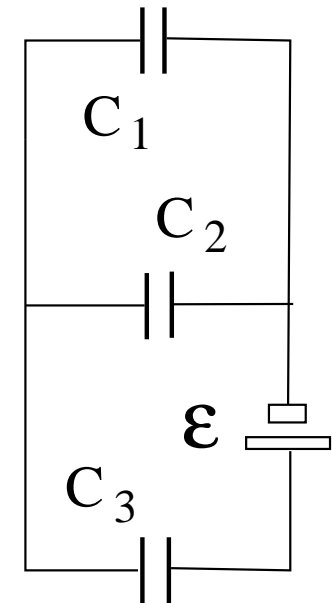- (a) Find the equivalent capacitance  $C_{eq}$ .
- (b) Find the charge  $Q_2$  on capacitor  $C_2$ .
- (c) Find the voltage  $V_3$  across capacitor  $C_3$ .
- (d) Find the total energy  $U$  stored in the capacitors.



## Unit Exam II: Problem #1 (Spring '18)



The circuit shown has reached equilibrium.

The specifications are  $\mathcal{E} = 12\text{V}$  [18V],  $C_1 = C_2 = C_3 = 5\text{nF}$  [4nF]

- (a) Find the equivalent capacitance  $C_{eq}$ .
- (b) Find the charge  $Q_2$  on capacitor  $C_2$ .
- (c) Find the voltage  $V_3$  across capacitor  $C_3$ .
- (d) Find the total energy  $U$  stored in the capacitors.

**Solution:**


(a)  $C_{12} = C_1 + C_2 = 10\text{nF}$  [8nF].

$$C_{eq} = \left( \frac{1}{C_{12}} + \frac{1}{C_3} \right)^{-1} = \frac{10}{3}\text{nF} \left[ \frac{8}{3}\text{nF} \right].$$

(b)  $Q_3 = Q_{12} = \mathcal{E}C_{eq} = 40\text{nC}$  [48nC],  $Q_1 = Q_2 = \frac{1}{2}Q_{12} = 20\text{nC}$  [24nC].

(c)  $V_3 = \frac{Q_3}{C_3} = 8\text{V}$  [12V],  $V_1 = V_2 = \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = 4\text{V}$  [6V].

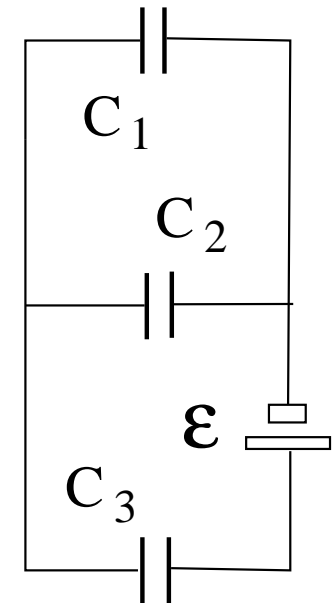(d)  $U = \frac{1}{2}C_{eq}\mathcal{E}^2 = 240\text{nJ}$  [432nJ].




## Unit Exam II: Problem #2 (Spring '18)



The circuit shown is in a steady state.

The specifications are  $\mathcal{E} = 12\text{V}$  [18V],  $R_1 = R_2 = R_3 = 5\Omega$  [4Ω].

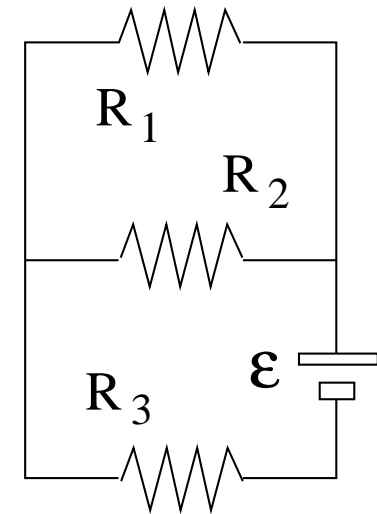- (a) Find the equivalent resistance  $R_{eq}$ .
- (b) Find the currents  $I_1$  through resistor  $R_1$ .
- (c) Find the voltage  $V_3$  across resistor  $R_3$ .
- (d) Find the power  $P$  produced by the battery.




## Unit Exam II: Problem #2 (Spring '18)



The circuit shown is in a steady state.

The specifications are  $\mathcal{E} = 12\text{V}$  [18V],  $R_1 = R_2 = R_3 = 5\Omega$  [4Ω].

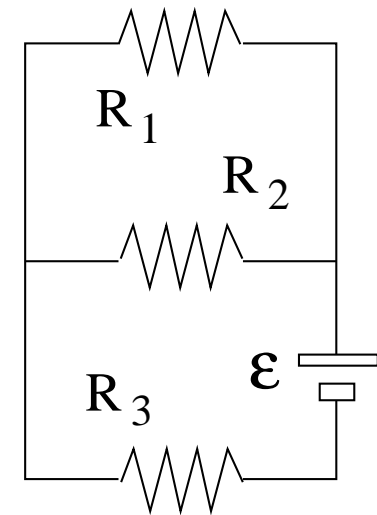- (a) Find the equivalent resistance  $R_{eq}$ .
- (b) Find the currents  $I_1$  through resistor  $R_1$ .
- (c) Find the voltage  $V_3$  across resistor  $R_3$ .
- (d) Find the power  $P$  produced by the battery.



**Solution:**

$$(a) \quad R_{12} = \left( \frac{1}{R_1} + \frac{1}{R_3} \right)^{-1} = 2.5\Omega \text{ [2.0}\Omega\text{]}, \quad R_{eq} = R_{12} + R_3 = 7.5\Omega \text{ [6.0}\Omega\text{]}.$$

$$(b) \quad I_3 = I_{12} = \frac{\mathcal{E}}{R_{eq}} = 1.6\text{A [3.0A]}, \quad I_1 = I_2 = \frac{1}{2}I_{12} = 0.8\text{A [1.5A]}.$$

$$(c) \quad V_3 = R_3 I_3 = 8\text{V [12V]}, \quad V_1 = V_2 = R_1 I_1 = R_2 I_2 = 4\text{V [6V]}.$$


$$(d) \quad P = \frac{\mathcal{E}^2}{R_{eq}} = R_{eq} I_3^2 = 19.2\text{W [54.0W]}.$$

## Unit Exam II: Problem #3 (Spring '18)



This circuit is in a steady state with the switch  $S$  either open or closed.

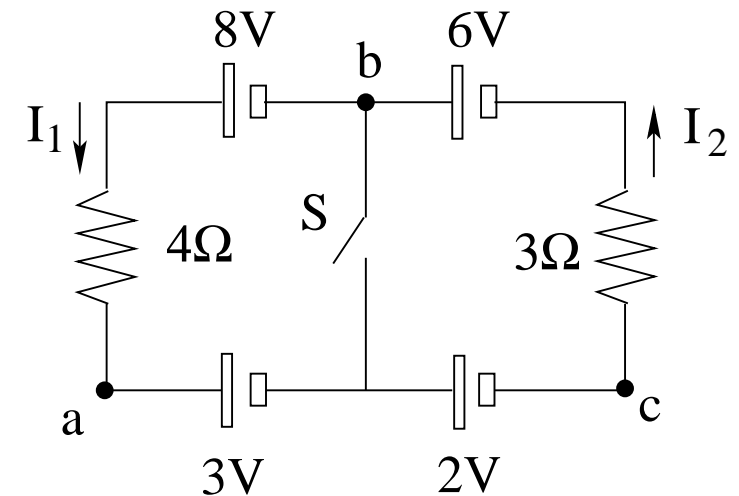- (a) Find the currents  $I_1$  and  $I_2$  when the switch is open.
- (b) Find the currents  $I_1$  and  $I_2$  when the switch is closed.
- (c) Find the voltages  $V_a - V_b$  and  $V_b - V_c$  when the switch is open.
- (d) Find the voltages  $V_a - V_b$  and  $V_b - V_c$  when the switch is closed.




## Unit Exam II: Problem #3 (Spring '18)



This circuit is in a steady state with the switch  $S$  either open or closed.

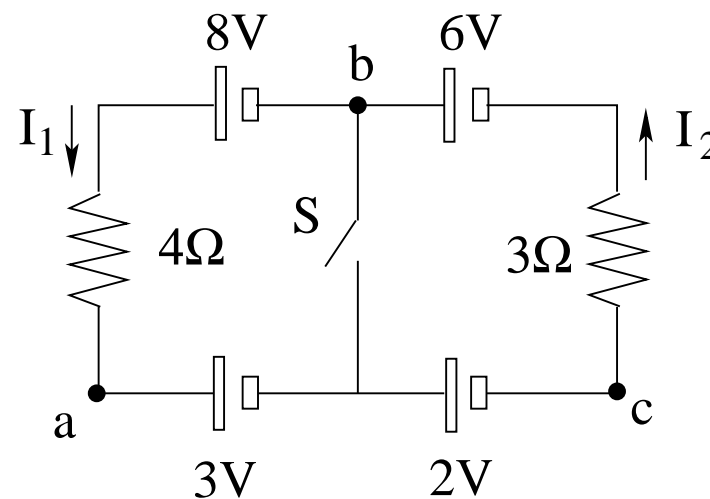- (a) Find the currents  $I_1$  and  $I_2$  when the switch is open.
- (b) Find the currents  $I_1$  and  $I_2$  when the switch is closed.
- (c) Find the voltages  $V_a - V_b$  and  $V_b - V_c$  when the switch is open.
- (d) Find the voltages  $V_a - V_b$  and  $V_b - V_c$  when the switch is closed.



**Solution:**

$$(a) \quad I_1 = I_2 = \frac{6V + 8V - 3V - 2V}{3\Omega + 4\Omega} = \frac{9}{7}A = 1.29A.$$

$$(b) \quad I_1 = \frac{8V - 3V}{4\Omega} = \frac{5}{4}A = 1.25A, \quad I_2 = \frac{6V - 2V}{3\Omega} = \frac{4}{3}A = 1.33A.$$

$$(c) \quad V_a - V_b = 8V - (1.29A)(4\Omega) = 2.84V, \quad V_b - V_c = 6V - (1.29A)(3\Omega) = 2.13V.$$

$$(d) \quad V_a - V_b = 3V, \quad V_b - V_c = 2V.$$