Unit Exam II: Problem #1 (Fall '18)



The circuit shown has reached equilibrium. The specifications are $\mathcal{E} = 12V$ [14V], $C_1 = C_2 = C_3 = 7nF$ [5nF]

- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the charges Q_1, Q_2, Q_3 on capacitors 1, 2, 3, respectively.
- (c) Find the voltages V_1, V_2, V_3 across capacitors 1, 2, 3, respectively.



Unit Exam II: Problem #1 (Fall '18)



The circuit shown has reached equilibrium.

The specifications are $\mathcal{E} = 12V$ [14V], $C_1 = C_2 = C_3 = 7nF$ [5nF]

- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the charges Q_1, Q_2, Q_3 on capacitors 1, 2, 3, respectively.
- (c) Find the voltages V_1, V_2, V_3 across capacitors 1, 2, 3, respectively.

Solution:

(a)
$$C_{13} = \left(\frac{1}{C_1} + \frac{1}{C_3}\right)^{-1} = \frac{7}{2} nF \left[\frac{5}{2} nF\right].$$

 $C_{eq} = C_{13} + C_2 = \frac{21}{2} nF \left[\frac{15}{2} nF\right].$
(b) $Q_1 = Q_3 = \mathcal{E}C_{13} = 42nC$ [35nC], $Q_2 = \mathcal{E}C_2 = 84nC$ [70nC].
(c) $V_1 = \frac{Q_1}{C_1} = 6V$ [7V], $V_2 = \frac{Q_2}{C_2} = 12V$ [14V], $V_3 = \frac{Q_3}{C_3} = 6V$ [7V].



Unit Exam II: Problem #2 (Fall '18)



The circuit shown is in a steady state. The specifications are $\mathcal{E} = 12V$ [14V], $R_1 = R_2 = R_3 = 7\Omega$ [5 Ω].

- (a) Find the equivalent resistance R_{eq} .
- (b) Find the currents I_1, I_2, I_3 through resistors 1, 2, 3, respectively.
- (c) Find the voltages V_1, V_2, V_3 across resistors 1, 2, 3, respectively.



Unit Exam II: Problem #2 (Fall '18)



The circuit shown is in a steady state. The specifications are $\mathcal{E} = 12V$ [14V], $R_1 = R_2 = R_3 = 7\Omega$ [5 Ω].

- (a) Find the equivalent resistance R_{eq} .
- (b) Find the currents I_1, I_2, I_3 through resistors 1, 2, 3, respectively.
- (c) Find the voltages V_1, V_2, V_3 across resistors 1, 2, 3, respectively.



Solution:

(a)
$$R_{13} = R_1 + R_3 = 14\Omega [10A], \quad R_{eq} = \left(\frac{1}{R_{13}} + \frac{1}{R_2}\right)^{-1} = 4.67\Omega [3.33A].$$

(b)
$$I_1 = I_3 = \frac{\mathcal{E}}{R_{13}} = 0.857 \text{A} [1.40 \text{A}], \quad I_2 = \frac{\mathcal{E}}{R_2} = 1.71 \text{A} [2.80 \text{A}].$$

(c) $V_1 = R_1 I_1 = 6V [7V], V_2 = R_2 I_2 = 12V [14V], V_3 = R_3 I_3 = 6V [7V].$

Unit Exam II: Problem #3 (Fall '18)



This circuit is in a steady state with the switch S either open or closed. The specifications are $\mathcal{E}_1 = 4V$ [3V], $\mathcal{E}_2 = 6V$ [7V], $\mathcal{E}_3 = 10V$ [9V], $R = 7\Omega$ [11 Ω].

- (a) Find the currents I_1 and I_2 when the switch is open.
- (b) Find the currents I_1 and I_2 when the switch is closed.
- (c) Find the voltages $V_b V_a$ when the switch is open.
- (d) Find the voltages $V_b V_a$ when the switch is closed.



Unit Exam II: Problem #3 (Fall '18)



This circuit is in a steady state with the switch *S* either open or closed. The specifications are $\mathcal{E}_1 = 4V$ [3V], $\mathcal{E}_2 = 6V$ [7V], $\mathcal{E}_3 = 10V$ [9V], $R = 7\Omega$ [11 Ω].

- (a) Find the currents I_1 and I_2 when the switch is open.
- (b) Find the currents I_1 and I_2 when the switch is closed.
- (c) Find the voltages $V_b V_a$ when the switch is open.
- (d) Find the voltages $V_b V_a$ when the switch is closed.

Solution:

(a)
$$I_1 = I_2 = \frac{10V - 4V}{7\Omega + 7\Omega} = 0.429A$$

 $\left[I_1 = I_2 = \frac{9V - 3V}{11\Omega + 11\Omega} = 0.273A\right]$
(b) $I_1 = \frac{6V - 4V}{7\Omega} = 0.286A, \quad I_2 = \frac{10V - 6V}{7\Omega} = 0.571A$
 $\left[I_1 = \frac{7V - 3V}{11\Omega} = 0.364A, \quad I_2 = \frac{9V - 7V}{11\Omega} = 0.182A\right]$
(c) $V_b - V_a = (0.429A)(7\Omega) + 4V = 10V - (0.429A)(7\Omega) = 7V$
 $\left[V_b - V_a = (0.273A)(11\Omega) + 3V = 9V - (0.273A)(11\Omega) = 6V\right]$
(d) $V_b - V_a = 6V$ $\left[V_b - V_a = 7V\right]$

